
 


AND GATE

 

| INPUT | | OUTPUT |
|-------|---|---------|
| A | B | A AND B |
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

VHDL CODES

=====
and_gate.vhdl
=====

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

-- Hendra Kesuma

```
entity and_ent is  
  Port ( and_in1 : in std_logic;  
        and_in2 : in std_logic;  
        and_out  : out std_logic);  
end and_ent;
```

```
architecture and_arch of and_ent is  
begin  
  process(and_in1, and_in2)  
  begin  
    if((and_in1='1') and (and_in2='1')) then  
      and_out<='1';  
    else  
      and_out<='0';  
    end if;  
  end process;  
end and_arch;
```

TESTBENCH CODE

=====
tb_and_ent.vhd
=====

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
USE ieee.numeric_std.ALL;
```

-- Hendra Kesuma


```

ENTITY tb_and_ent IS
END tb_and_ent;






ARCHITECTURE tb_and_arch OF tb_and_ent IS
  COMPONENT and_ent
  PORT(
    and_in1 : IN std_logic;
    and_in2 : IN std_logic;
    and_out : OUT std_logic
  );
  END COMPONENT;
  FOR uut:and_ent use entity work.and_ent(tb_and_arch);
    SIGNAL and_in1 : std_logic;
    SIGNAL and_in2 : std_logic;
    SIGNAL and_out : std_logic;
  BEGIN
    and_in1 <= '0' after 5 ns, '1' after 25 ns;
    and_in2 <= '0' after 0 ns, '1' after 15 ns, '0' after 35 ns;
    uut:and_ent port map(and_in1, and_in2, and_out);
  end tb_and_arch;

```

SIMULATION

 

OR GATE

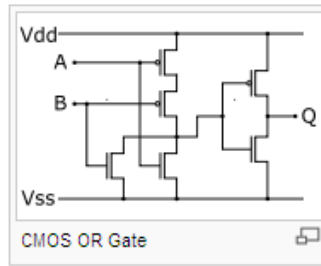    

| INPUT | | OUTPUT |
|-------|---|--------|
| A | B | A + B |
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

VHDL CODE

```
=====
or_gate.vhdl
=====
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
-- Hendra Kesuma
```

```
entity or_ent is
  Port ( or_in1 : in std_logic;
        or_in2 : in std_logic;
        or_out  : out std_logic);
end or_ent;
```

```
architecture or_arch of or_ent is
begin
  process(or_in1,or_in2)
  begin
    if((or_in1='0') and (or_in2='0')) then
      or_out<='0';
    else
      or_out<='1';
    end if;
  end process;
end or_arch;
```

TESTBENCH CODE

```
=====
tb_or_ent.vhd
=====
```

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
```


```
-- Hendra Kesuma
```

```




ENTITY tb_or_ent IS
END tb_or_ent;
ARCHITECTURE tb_or_arch OF tb_or_ent IS
  COMPONENT or_ent
  PORT(
    or_in1 : IN std_logic;
    or_in2 : IN std_logic;
    or_out : OUT std_logic
  );
  END COMPONENT;
  FOR uut:or_ent use entity work.or_ent(or_arch);
  SIGNAL or_in1 : std_logic;
  SIGNAL or_in2 : std_logic;
  SIGNAL or_out : std_logic;
BEGIN
  or_in1<='0' after 5 ns, '1' after 25 ns;
  or_in2<='0' after 0 ns, '1' after 15 ns, '0' after 35 ns;
  uut:or_ent port map(or_in1, or_in2, or_out);
end tb_or_arch;

```


SIMULATION

 


NOT GATE

   


NMOS Inverter

 

PMOS Inverter

 

Static CMOS Inverter

 

Schematic of a Saturated-Load Digital Inverter

| INPUT | OUTPUT |
|-------|--------|
| A | NOT A |
| 0 | 1 |
| 1 | 0 |

VHDL CODE

```
not_Gate.vhdl
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
-- Hendra Kesuma
```

```
entity not_ent is
    Port ( not_in : in std_logic;
          not_out : out std_logic);
end not_ent;
```

```
architecture not_arch of not_ent is
begin
    process(not_in)
    begin
        if(not_in='1') then
            not_out<='0';
        else
            not_out<='1';
        end if;
    end process;
end not_arch;
```

TESTBENCH CODE


```
=====
tb_not_ent.vhd
=====
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

-- Hendra Kesuma


ENTITY tb_not_ent IS
END tb_not_ent;

ARCHITECTURE tb_not_arch OF tb_not_ent IS
    COMPONENT not_ent
    PORT(
        not_in : IN std_logic;
        not_out : OUT std_logic
    );
    END COMPONENT;
    FOR uut: not_ent use entity work.not_ent(not_arch);
        SIGNAL not_in : std_logic;
        SIGNAL not_out : std_logic;
BEGIN
    not_in <= '0' after 5 ns, '1' after 10 ns, '0' after 20 ns;
    uut: not_ent port map(not_in, not_out);
end tb_not_arch;
```

SIMULATION

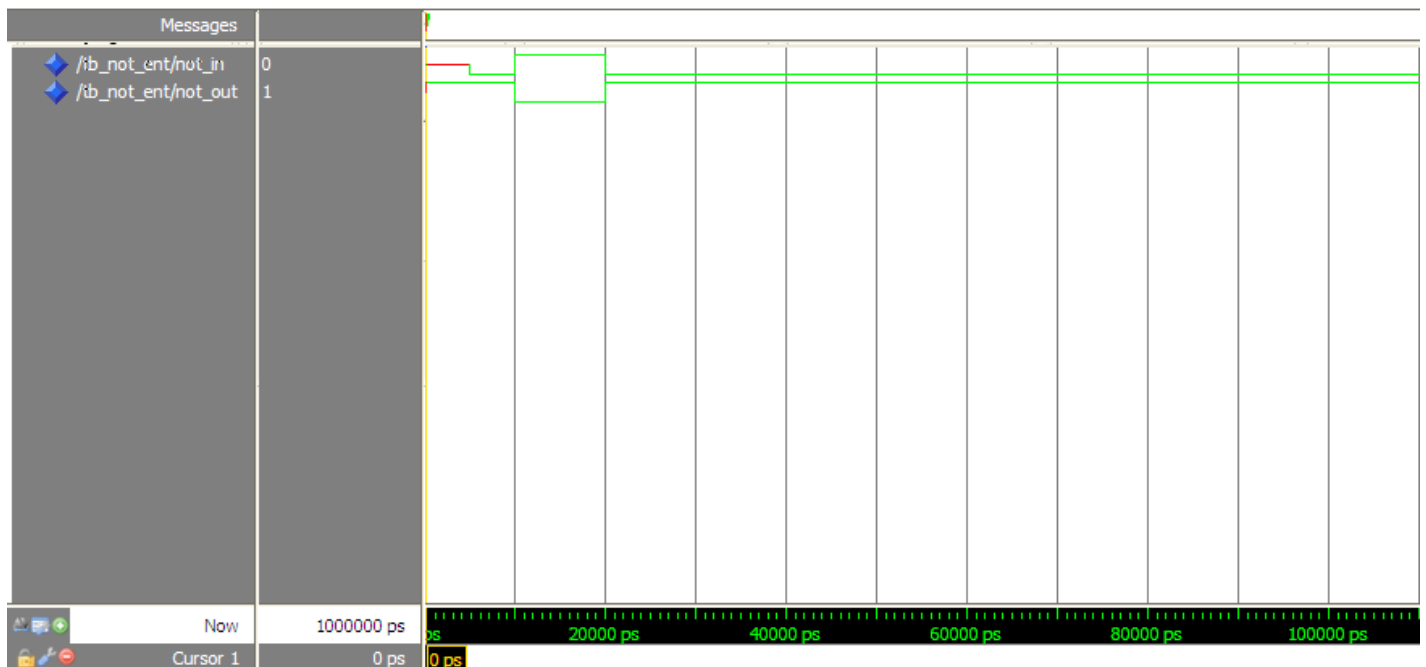

Driver(BUFFER)

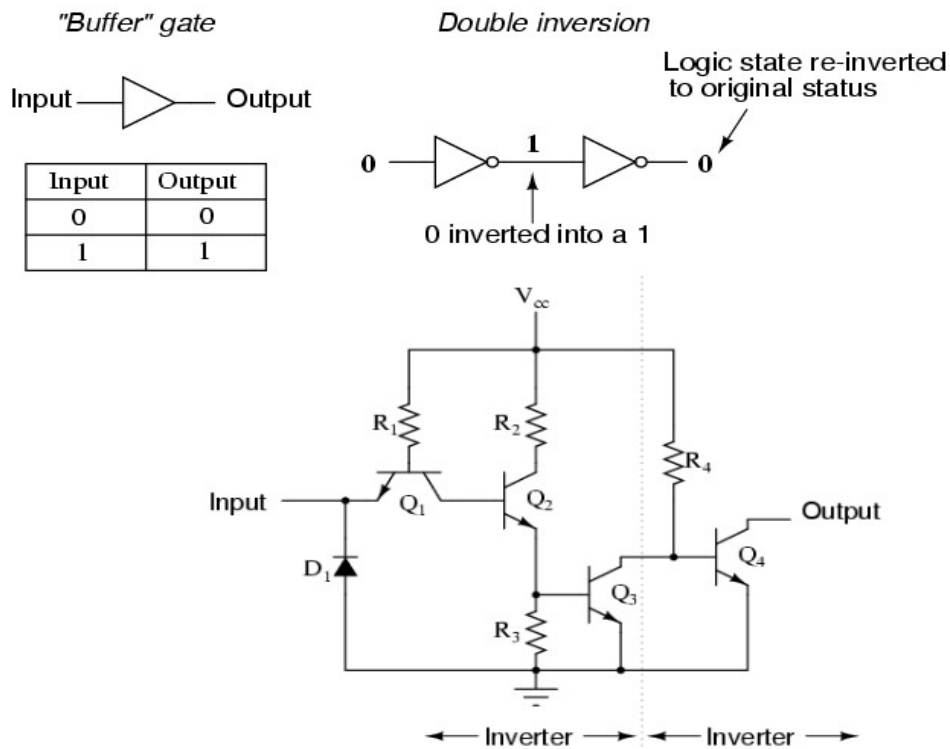

VHDL CODE

```
=====
driver_Gate.vhdl
=====
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
-- Hendra Kesuma
```

```
entity driver_ent is
  Port ( driver_in : in std_logic;
        driver_out : out std_logic);
end driver_ent;
```

```
architecture driver_arch of driver_ent is
begin
  driver_out <= driver_in after 5 ns;
end driver_arch;
```

TESTBENCH CODE


```
=====
tb_driver_ent.vhd
=====
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

-- Hendra Kesuma


ENTITY tb_driver_ent IS
END tb_driver_ent;

ARCHITECTURE tb_driver_arch OF tb_driver_ent IS
    COMPONENT driver_ent
    PORT(
        driver_in : IN std_logic;
        driver_out : OUT std_logic
    );
    END COMPONENT;
    FOR uut:driver_ent use entity work.driver_ent(driver_arch);
        SIGNAL driver_in : std_logic;
        SIGNAL driver_out : std_logic;
BEGIN
    driver_in<='0' after 5 ns, '1' after 10 ns, '0' after 20 ns;
    uut:driver_ent port map(driver_in, driver_out);
END tb_driver_arch;
```

SIMULATION

 

NAND GATE

 

VHDL CODE (using *if-else-then* statement)

```
=====
nand_gate_if.vhdl
=====
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Hendra Kesuma

entity nand_ent_if is
    Port ( nand_in1_if : in std_logic;
          nand_in2_if : in std_logic;
          nand_out_if  : out std_logic);
end nand_ent_if;

architecture nand_arch_if of nand_ent_if is
begin
    process(nand_in1_if,nand_in2_if)
    begin
        if((nand_in1_if='1') and (nand_in2_if='1')) then
            nand_out_if<='0';
        else
            nand_out_if<='1';
        end if;
    end process;
end nand_arch_if;
```

TESTBENCH CODE

```
=====
tb_nand_ent_if.vhd
=====
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

-- Hendra Kesuma


ENTITY tb_nand_ent_if IS
END tb_nand_ent_if;
```

ARCHITECTURE tb_nand_arch_if OF tb_nand_ent_if IS

```
    COMPONENT nand_ent_if
    PORT(
        nand_in1_if : IN std_logic;
        nand_in2_if : IN std_logic;
        nand_out_if : OUT std_logic
    );
    END COMPONENT;
    FOR uut:nand_ent_if use entity work.nand_ent_if(nand_arch_if);
        SIGNAL nand_in1_if : std_logic;
        SIGNAL nand_in2_if : std_logic;
        SIGNAL nand_out_if : std_logic;

    BEGIN
        nand_in1_if<='0' after 5 ns, '1' after 25 ns;
        nand_in2_if<='0' after 0 ns, '1' after 15 ns, '0' after 35 ns;
        uut:nand_ent_if port map(nand_in1_if, nand_in2_if, nand_out_if);
    end tb_nand_arch_if;
```

SIMULATION

 

VHDL CODE (using *case-when* statement)

```
nand_Gate_case.vhdl
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
-- Hendra Kesuma
```

```

entity nand_ent_case is
  Port ( nand_in1_case : in std_logic;
        nand_in2_case : in std_logic;
        nand_out_case : out std_logic);
end nand_ent_case;
architecture nand_arch_case of nand_ent_case is
begin
  process(nand_in1_case, nand_in2_case)
    variable Temp_variable : std_logic_vector (1 downto 0);
  begin
    Temp_variable := (nand_in1_case & nand_in2_case);
    case Temp_variable is
      when "00" => nand_out_case <= '1';
      when "10" => nand_out_case <= '1';
      when "01" => nand_out_case <= '1';
      when "11" => nand_out_case <= '0';
      when others => nand_out_case <= 'U';
    end case;
  end process;
end nand_arch_case;

```

TESTBENCH CODE

```

=====
tb_nand_ent_case.vhd
=====

```

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

```

```

-- Hendra Kesuma

```

```

ENTITY tb_nand_ent_case IS
END tb_nand_ent_case;

```

```

ARCHITECTURE tb_nand_arch_case OF tb_nand_ent_case IS

```

```

  COMPONENT nand_ent_case
  PORT(
    nand_in1_case : IN std_logic;
    nand_in2_case : IN std_logic;
    nand_out_case : OUT std_logic
  );

```

```

  END COMPONENT;

```

```

  FOR uut:nand_ent_case use entity work.nand_ent_case(nand_arch_case);
    SIGNAL nand_in1_case : std_logic;
    SIGNAL nand_in2_case : std_logic;
    SIGNAL nand_out_case : std_logic;

```

```

BEGIN

```

```

  nand_in1_case<='0' after 5 ns, '1' after 25 ns;
  nand_in2_case<='0' after 0 ns, '1' after 15 ns, '0' after 35 ns;
  uut:nand_ent_case port map(nand_in1_case, nand_in2_case, nand_out_case);


```

```


end tb_nand_arch_case;

```

SIMULATION

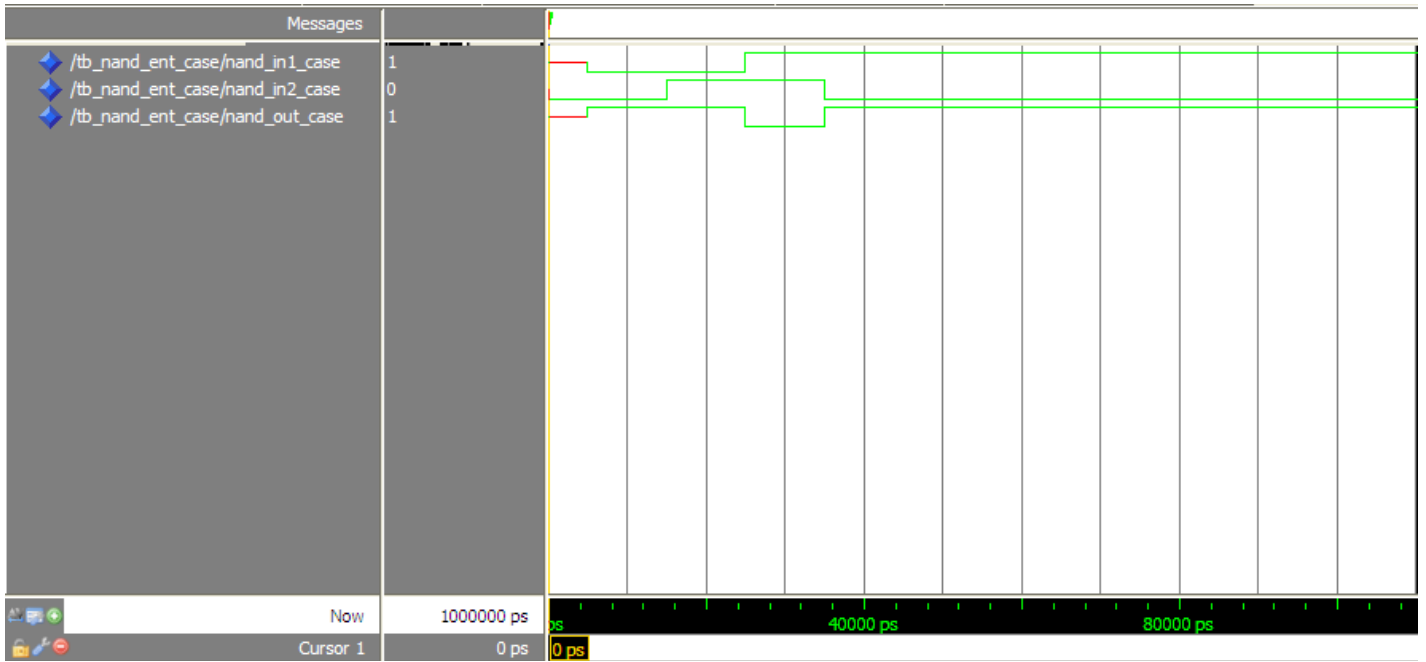

NOR GATE

 

| Input A | Input B | Output Q |
|---------|---------|----------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

VHDL CODE (using *if-else-then* statement)

```
nor_gate_if.vhdl
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
-- Hendra Kesuma
```

```
entity nor_ent_if is
  Port ( nor_in1_if : in std_logic;
        nor_in2_if : in std_logic;
        nor_out_if : out std_logic);
end nor_ent_if;
```

```

architecture nor_arch_if of nor_ent_if is
begin
  process(nor_in1_if,nor_in2_if)
  begin
    if((nor_in1_if='0') and (nor_in2_if='0')) then
      nor_out_if<='1';
    else
      nor_out_if<='0';
    end if;
  end process;
end nor_arch_if;

```

TESTBENCH CODE

```

=====
tb_nor_ent_if.vhd
=====

```

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

```

```

-- Hendra Kesuma

```

```

ENTITY tb_nor_ent_if IS
END tb_nor_ent_if;

```

```

ARCHITECTURE tb_nor_arch_if OF tb_nor_ent_if IS
  COMPONENT nor_ent_if
  PORT(
    nor_in1_if : IN std_logic;
    nor_in2_if : IN std_logic;
    nor_out_if : OUT std_logic
  );
  END COMPONENT;
  FOR uut:nor_ent_if use entity work.nor_ent_if(nor_arch_if);
  SIGNAL nor_in1_if : std_logic;
  SIGNAL nor_in2_if : std_logic;
  SIGNAL nor_out_if : std_logic;


```

```

BEGIN
  nor_in1_if<='0' after 5 ns, '1' after 25 ns;
  nor_in2_if<='0' after 0 ns, '1' after 15 ns, '0' after 35 ns;
  uut:nor_ent_if port map(nor_in1_if, nor_in2_if, nor_out_if);
end tb_nor_arch_if;

```

SIMULATION

 

VHDL CODE (using *case-when* statement)

```
nor_Gate_case.vhdl
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Hendra Kesuma

entity nor_ent_case is
  Port ( nor_in1_case : in std_logic;
        nor_in2_case : in std_logic;
        nor_out_case  : out std_logic);
end nor_ent_case;

architecture nor_arch_case of nor_ent_case is
begin
  process(nor_in1_case, nor_in2_case)
    variable Temp_variable : std_logic_vector (1 downto 0);
  begin
    Temp_variable := (nor_in1_case & nor_in2_case);
    case Temp_variable is
      when "00" => nor_out_case <= '1';
      when "10" => nor_out_case <= '0';
      when "01" => nor_out_case <= '0';
      when "11" => nor_out_case <= '0';
      when others => nor_out_case <= 'U';
    end case;
  end process;
end nor_arch_case;
```

TESTBENCH CODE

```
tb_nor_ent_case.vhd
```

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
USE ieee.numeric_std.ALL;
```

```
-- Hendra Kesuma
```

```
ENTITY tb_nor_ent_case IS  
END tb_nor_ent_case;
```

```
ARCHITECTURE tb_nor_arch_case OF tb_nor_ent_case IS
```

```
    COMPONENT nor_ent_case  
    PORT(  
        nor_in1_case : IN std_logic;  
        nor_in2_case : IN std_logic;  
        nor_out_case : OUT std_logic  
    );
```

```
END COMPONENT;
```

```
FOR uut:nor_ent_case use entity work.nor_ent_case(nor_arch_case);  
    SIGNAL nor_in1_case : std_logic;  
    SIGNAL nor_in2_case : std_logic;  
    SIGNAL nor_out_case : std_logic;
```

```
BEGIN
```


```
    nor_in1_case<='0' after 5 ns, '1' after 25 ns;
```

```
    nor_in2_case<='0' after 0 ns, '1' after 15 ns, '0' after 35 ns;
```



```
    uut:nor_ent_case port map(nor_in1_case, nor_in2_case, nor_out_case);
```

```
end tb_nor_arch_case;
```

SIMULATION

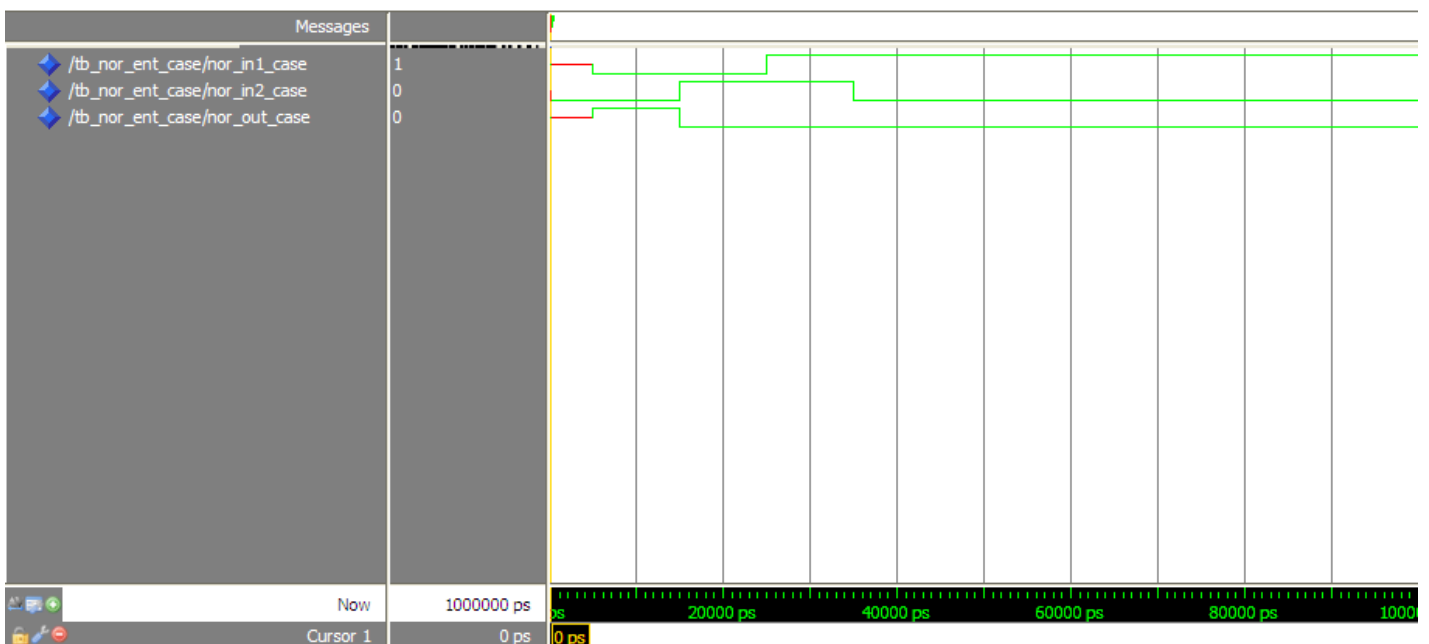

XOR GATE

  

| Input A | Input B | Output Q |
|---------|---------|----------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

VHDL CODE (using *if-else-then* statement)

```
=====  
xor_gate_if.vhdl  
=====  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;  
  
-- Hendra Kesuma  
  
entity xor_ent_if is  
    Port ( xor_in1_if : in std_logic;  
          xor_in2_if : in std_logic;  
          xor_out_if  : out std_logic);  
end xor_ent_if;  
  
architecture xor_arch_if of xor_ent_if is  
begin  
    process(xor_in1_if,xor_in2_if)  
    begin  
        if((xor_in1_if='0') and (xor_in2_if='0')) then  
            xor_out_if<='0';  
        elsif((xor_in1_if='1') and (xor_in2_if='1')) then  
            xor_out_if<='0';  
        else  
            xor_out_if<='1';  
        end if;  
    end process;  
end xor_arch_if;
```

TESTBENCH CODE


```
=====  
tb_xor_ent_if.vhd  
=====  
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
USE ieee.numeric_std.ALL;  
  
-- Hendra Kesuma  
  
ENTITY tb_xor_ent_if IS  
END tb_xor_ent_if;
```


ARCHITECTURE tb_xor_arch_if OF tb_xor_ent_if IS

```
    COMPONENT xor_ent_if
    PORT(
        xor_in1_if : IN std_logic;
        xor_in2_if : IN std_logic;
        xor_out_if : OUT std_logic
    );
    END COMPONENT;
    FOR uut:xor_ent_if use entity work.xor_ent_if(xor_arch_if);
        SIGNAL xor_in1_if : std_logic;
        SIGNAL xor_in2_if : std_logic;
        SIGNAL xor_out_if : std_logic;

    BEGIN
        xor_in1_if<='0' after 5 ns, '1' after 25 ns;
        xor_in2_if<='0' after 0 ns, '1' after 15 ns, '0' after 35 ns;
        uut:xor_ent_if port map(xor_in1_if, xor_in2_if, xor_out_if);
    end tb_xor_arch_if;
```

SIMULATION

 

VHDL CODE (using *case-when* statement)

```
=====  
xor_Gate_case.vhdl  
=====
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
-- Hendra Kesuma
```

```

entity xor_ent_case is
  Port ( xor_in1_case : in std_logic;
        xor_in2_case : in std_logic;
        xor_out_case  : out std_logic);
end xor_ent_case;

architecture xor_arch_case of xor_ent_case is
begin
  process(xor_in1_case, xor_in2_case)
    variable Temp_variable : std_logic_vector (1 downto 0);
  begin
    Temp_variable := (xor_in1_case & xor_in2_case);
    case Temp_variable is
      when "00" => xor_out_case <= '0';
      when "10" => xor_out_case <= '1';
      when "01" => xor_out_case <= '1';
      when "11" => xor_out_case <= '0';
      when others => xor_out_case <= 'U';
    end case;
  end process;
end xor_arch_case;

```

TESTBENCH CODE

```

=====
tb_xor_ent_case.vhd
=====

```

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

```

```

-- Hendra Kesuma

```

```

ENTITY tb_xor_ent_case IS
END tb_xor_ent_case;

```

```

ARCHITECTURE tb_xor_arch_case OF tb_xor_ent_case IS

```

```

  COMPONENT xor_ent_case
  PORT(
    xor_in1_case : IN std_logic;
    xor_in2_case : IN std_logic;
    xor_out_case : OUT std_logic
  );

```

```

  END COMPONENT;

```

```

  FOR uut:xor_ent_case use entity work.xor_ent_case(xor_arch_case);
    SIGNAL xor_in1_case : std_logic;
    SIGNAL xor_in2_case : std_logic;
    SIGNAL xor_out_case : std_logic;

```

```

BEGIN

```

```

  xor_in1_case<='0' after 5 ns, '1' after 25 ns;
  xor_in2_case<='0' after 0 ns, '1' after 15 ns, '0' after 35 ns;
  uut:xor_ent_case port map(xor_in1_case, xor_in2_case, xor_out_case);
end tb_xor_arch_case;

```

SIMULATION

