 



## Adder

A half adder can add two bits. It has two inputs, generally labeled **A** and **B**, and two outputs, the sum **S** and carry **C**. **S** is the two-bit **XOR** of **A** and **B**, and **C** is the **AND** of **A** and **B**. Essentially the output of a half adder is the sum of two one-bit numbers, with **C** being the most significant of these two outputs.

A **full adder** is capable of adding three bits: two bits and one carry bit. It has three inputs - **A**, **B**, and carry **C**, such that multiple full adders can be used to add larger numbers. To remove ambiguity between the input and output carry lines, the carry in is labelled **C<sub>i</sub>** or **C<sub>in</sub>** while the carry out is labelled **C<sub>o</sub>** or **C<sub>out</sub>**.




Half Adder

 

Full Adder

## Full Adder

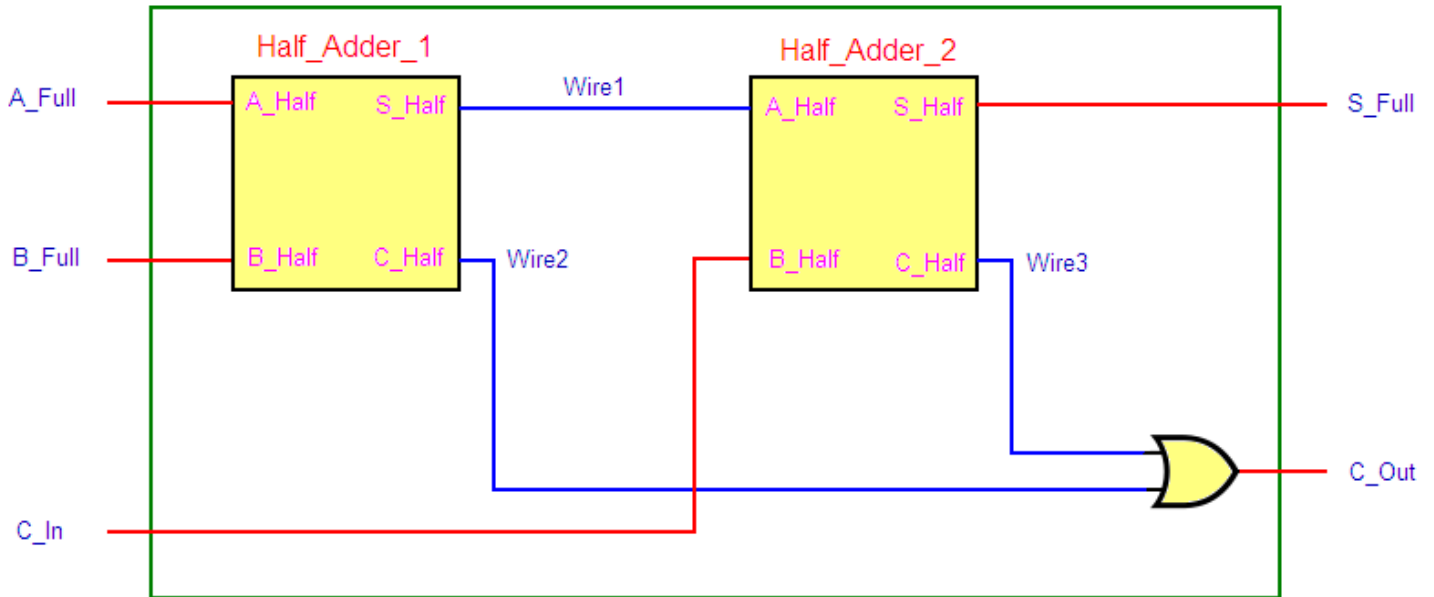

### VHDL CODE

=====  
H\_Adder.vhdl  
=====

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

-- Hendra Kesuma

```
entity Half_Adder_ent is  
  Port ( A_Half : in std_logic;  
        B_Half : in std_logic;  
        S_Half  : out std_logic;  
        C_Half  : out std_logic);  
end Half_Adder_ent;
```

```
architecture Half_Adder_arch of Half_Adder_ent is  
begin  
  process(A_Half, B_Half)  
  begin  
    S_Half <= (A_Half xor B_Half);  
    C_Half <= (A_Half and B_Half);  
  end process;  
end Half_Adder_arch;
```

## VHDL CODE

```
=====
Full_Adder.vhdl
=====
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
-- Hendra Kesuma
```

```
entity Full_Adder_ent is
  Port ( A_Full : in std_logic;
        B_Full : in std_logic;
        C_In : in std_logic;
        S_Full : out std_logic;
        C_Out : out std_logic);
end Full_Adder_ent;
```

```
architecture Full_Adder_arch of Full_Adder_ent is
```

```
  component Half_Adder_ent
  port(
    A_Half : in std_logic;
    B_Half : in std_logic;
    S_Half : out std_logic;
    C_Half : out std_logic);
  end component;
```

```
  signal Wire1 : std_logic;
  signal Wire2 : std_logic;
  signal Wire3 : std_logic;
```

```
begin
  Half_Adder_1: Half_Adder_ent
  port map(
    A_Half => A_Full,
    B_Half => B_Full,
    S_Half => Wire1,
    C_Half => Wire2
  );
```

```
  Half_Adder_2: Half_Adder_ent
  port map(
    A_Half => Wire1,
    B_Half => C_In,
    S_Half => S_Full,
    C_Half => Wire3
  );
```

```
C_Out <= (Wire3 or Wire2);  
end Full_Adder_arch;
```

## TESTBENCH CODE

```
=====
```

```
tb_Full_Adder.vhd
```

```
=====
```

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
USE ieee.numeric_std.ALL;
```

```
-- Hendra Kesuma
```

```
ENTITY full_adder_ent_tb_Full_Adder_vhd_tb IS  
END full_adder_ent_tb_Full_Adder_vhd_tb;
```

```
ARCHITECTURE behavior OF full_adder_ent_tb_Full_Adder_vhd_tb IS
```

```
    COMPONENT full_adder_ent  
    PORT(  
        A_Full : IN std_logic;  
        B_Full : IN std_logic;  
        C_In : IN std_logic;  
        S_Full : OUT std_logic;  
        C_Out : OUT std_logic  
    );  
END COMPONENT;
```

```
SIGNAL A_Full : std_logic;  
SIGNAL B_Full : std_logic;  
SIGNAL C_In : std_logic;  
SIGNAL S_Full : std_logic;  
SIGNAL C_Out : std_logic;
```

```
BEGIN
```

```
    uut: full_adder_ent PORT MAP(  
        A_Full => A_Full,  
        B_Full => B_Full,  
        C_In => C_In,  
        S_Full => S_Full,  
        C_Out => C_Out  
    );
```

```
-- *** Test Bench - User Defined Section ***
```

```

tb : PROCESS
BEGIN
A_Full <= '0' after 0 ns,
      '1' after 10 ns,
      '0' after 20 ns,
      '1' after 30 ns,
      '0' after 40 ns ;

B_Full <= '0' after 0 ns,
      '1' after 5 ns,
      '0' after 10 ns,
      '1' after 15 ns,
      '0' after 20 ns,
      '1' after 25 ns,
      '0' after 30 ns,
      '1' after 35 ns,
      '0' after 40 ns;


C_In  <= '0' after 0 ns,
      '1' after 20 ns;

wait; -- will wait forever
END PROCESS;
-- *** End Test Bench - User Defined Section ***


END;

```

### RTL Schematic

 

## SIMULATION

 

## RTL Schematic

