 


Data or Delay (D-Type) flip-flop

Data or Delay (**D-Type**) flip-flop have a single input line (**D**), instead of two input lines as the case of **RS** and **JK** flip-flops. The **D-Type** flip-flop is shown below.



In **D-Type** of flip-flop whatever input is applied to **D** will be transferred to the **Q** output as soon as the clock goes high, provided that the reset is not active, (*i.e reset is low = 0*). The **Q** output will be immediately reset to **0** irrespective of the low or high data in **D**-input if reset is active (*i.e reset is high = 1*). The truth table for **D-Type** of flip-flop is given below.

Reset (R)	Not Reset (NR)	Data (D)	Clock (CLK)	Output (Q)	Not Output (NQ)
1	0	X	X	0	1
0	1	0	(CLK = '1' and CLK 'event)	0	1
0	1	1	(CLK = '1' and CLK 'event)	1	0

VHDL CODE

```
=====
D_FF.vhdl
=====
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
-- Hendra Kesuma;
```

```
entity D_FF_ent is
  Port ( D : in STD_LOGIC;
        CLK : in STD_LOGIC;
        RN : in STD_LOGIC;
        Q : out STD_LOGIC;
        QN : out STD_LOGIC);
end D_FF_ent;
```

```

architecture D_FF_arch of D_FF_ent is
begin
  process(CLK, RN)
  begin
    if RN = '0' then
      Q <= '0';
      QN <= '1';
    elsif (RN = '1' and CLK = '1' and clk'event) then
      Q <= D;
      QN <= not D;
    end if;
  end process;
end D_FF_arch;

```

TESTBENCH CODE

```

=====
TB_D_FF.vhd
=====

```

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.all;
USE ieee.numeric_std.ALL;

```

-- Hendra Kesuma

```

ENTITY TB_D_FF_vhd IS
END TB_D_FF_vhd;

```

```

ARCHITECTURE behavior OF TB_D_FF_vhd IS

```

```

  -- Component Declaration for the Unit Under Test (UUT)

```

```

  COMPONENT D_FF_ent
  PORT(
    D : IN std_logic;
    CLK : IN std_logic;
    RN : IN std_logic;
    Q : OUT std_logic;
    QN : OUT std_logic
  );
  END COMPONENT;

```

```

  --Inputs

```

```

  SIGNAL D : std_logic := '0';
  SIGNAL CLK : std_logic := '0';
  SIGNAL RN : std_logic := '0';

```

```

  --Outputs

```

```

  SIGNAL Q : std_logic;

```

```

SIGNAL QN : std_logic;

BEGIN
-- Instantiate the Unit Under Test (UUT)
 uut: D_FF_ent
  PORT MAP(
    D => D,
    CLK => CLK,
    RN => RN,
    Q => Q,
    QN => QN
  );

tb1 : PROCESS
BEGIN
  -- Wait 100 ns for global reset to finish
  -- wait for 100 ns;

  -- Place stimulus here
  D <= '0' after 0 ns,
    '1' after 3 ns, '0' after 8 ns,
    '1' after 18 ns, '0' after 33 ns,
    '1' after 38 ns, '0' after 43 ns,
    '1' after 48 ns;

  RN <= '0' after 0 ns, '1' after 2 ns, '0' after 45 ns;

  wait; -- will wait forever

END PROCESS;

tb2 : PROCESS
BEGIN

  loop
  CLK <= '0';
  wait for 5 ns;
  CLK <= '1';
  wait for 5 ns;
  end loop;


  wait; -- will wait forever

END PROCESS;

END;


```

SIMULATION

 

Frequency Divider with (D-Type) flip-flop

 Data or Delay (**D-Type**) can be used to divide the clock input frequency by two, by connecting the **QN** output to the **D** input as shown in the figure below..



VHDL CODE

```
=====  
CLK_DIV.vhdl  
=====
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
-- Hendra Kesuma
```

```
entity CLK_DIV_ent is  
  Port ( CLK_IN : in  STD_LOGIC;  
         RN_IN  : in  STD_LOGIC;  
         CLK_OUT : out STD_LOGIC);  
end CLK_DIV_ent;
```

```
architecture CLK_DIV_arch of CLK_DIV_ent is
```

```
  component D_FF_ent  
    Port ( D : in  STD_LOGIC;  
          CLK : in  STD_LOGIC;  
          RN : in  STD_LOGIC;  
          Q : out STD_LOGIC;  
          QN : out STD_LOGIC);  
  end component;
```

```
  signal Wire1 : std_logic;
```

```
begin
```

```
  CLK_DIV: D_FF_ent  
  port map(  
    D => Wire1,  
    CLK => CLK_IN,  
    RN => RN_IN,  
    Q => CLK_OUT,  
    QN => Wire1 );
```

```
end CLK_DIV_arch;
```

TESTBENCH CODE

```
=====
TB_CLK_DIV.vhd
=====
```

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.all;
USE ieee.numeric_std.ALL;
```

```
-- Hendra Kesuma
```

```
ENTITY TB_CLK_DIV_vhd IS
END TB_CLK_DIV_vhd;
```

```
ARCHITECTURE behavior OF TB_CLK_DIV_vhd IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT CLK_DIV_ent
PORT(
    CLK_IN : IN std_logic;
    RN_IN : IN std_logic;
    CLK_OUT : OUT std_logic
);
END COMPONENT;
```

```
--Inputs
```

```
SIGNAL CLK_IN : std_logic := '0';
SIGNAL RN_IN : std_logic := '0';
```

```
--Outputs
```

```
SIGNAL CLK_OUT : std_logic;
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
 uut: CLK_DIV_ent PORT MAP(
    CLK_IN => CLK_IN,
    RN_IN => RN_IN,
    CLK_OUT => CLK_OUT
);
```

```
tb1 : PROCESS
```

```
BEGIN
```

```
-- Wait 100 ns for global reset to finish
-- wait for 100 ns;
```

```
-- Place stimulus here
```

```
RN_IN <= '0' after 0 ns, '1' after 2 ns, '0' after 60 ns;
```

```
wait; -- will wait forever
```

```
END PROCESS;
```

```
tb2 : PROCESS  
BEGIN
```

```
    loop  
        CLK_IN <= '0';  
        wait for 5 ns;  
        CLK_IN <= '1';  
        wait for 5 ns;  
    end loop;
```

```
    wait; -- will wait forever
```

```
END PROCESS;
```

```
END;
```

SIMULATION

